



LGS GROUP OF COLLEGES

A PROJECT OF LAHORE GRAMMAR SCHOOL

Sheet # _____

Name: Zymal Tariq
Subject: Physics


Class: FSc premedical Roll No. _____
Test No. WT8 Date: 20/11/24
Assignment

A	B	C	D	A	B	C	D	A	B	C	D	A	B	C	D	Marks Obtained
1				6				11				16				
2				7				12				17				
3				8				13				18				
4				9				14				19				
5				10				15				20				

Assignment

(Question #1)

$$\underline{(V_- \approx V_+)}$$

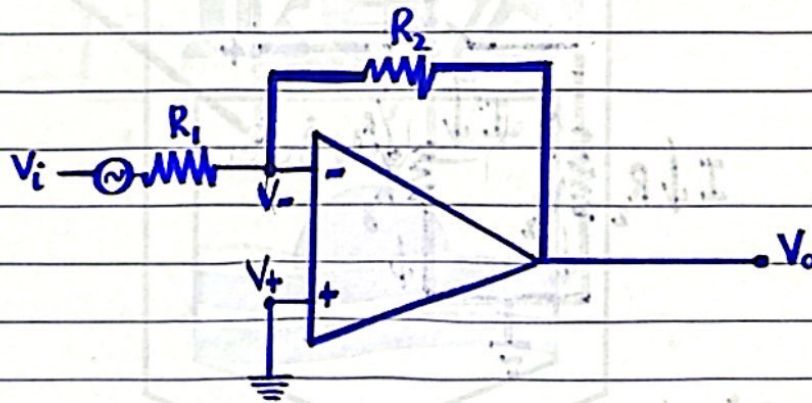

Proof:

Consider an operational amplifier V_+ as grounded,
So, $V_+ \approx 0$,

Also using, $A_{OL} = \frac{V_o}{V_+ - V_-} \Rightarrow V_+ - V_- = \frac{V_o}{A_{OL}}$

$$V_+ - V_- = \frac{V_o}{10^5} = \frac{V_o}{\text{very high value}} \approx 0 \text{ So, } V_+ - V_- \approx 0$$


$V_+ \approx V_-$ or $V_- \approx V_+$, So, V_+ is particularly grounded
and V_- is virtually grounded because of its equality with V_+ .



(Question #2)

(Opamp as Night Switch)

Circuit diagram:

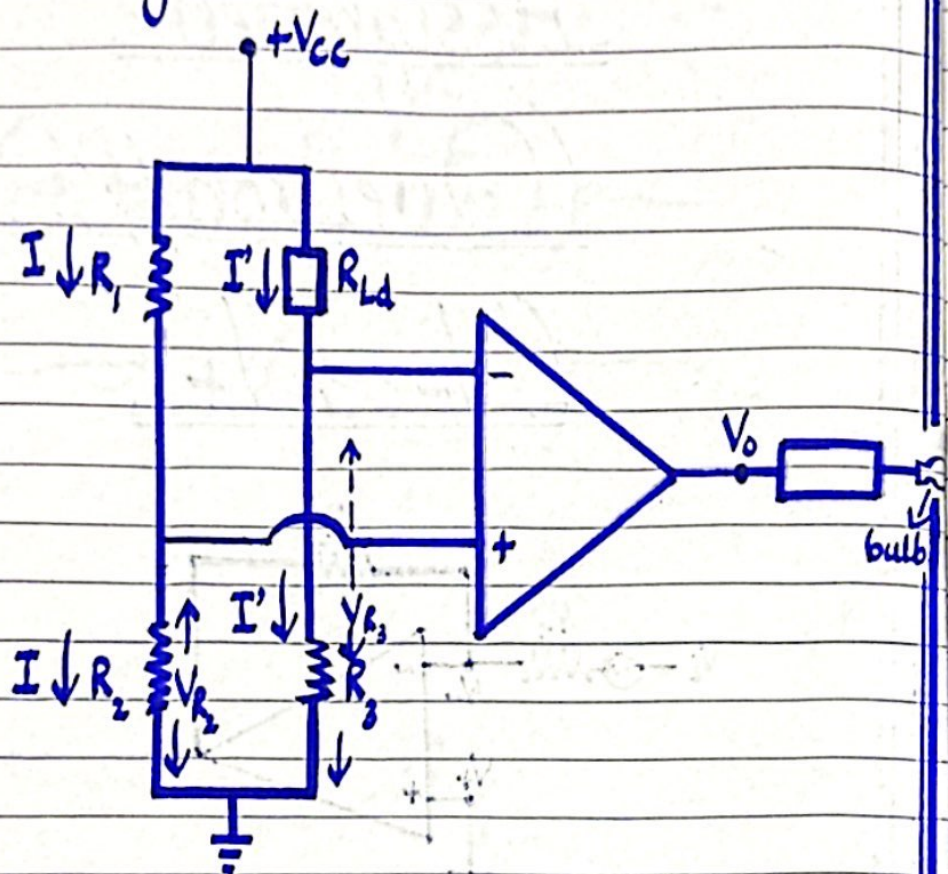

Expressions:

$$V_+ = V_{R_2}$$

$$V_{R_2} = (\text{Current through})(\text{resistance})$$

$$V_{R_2} = (I)(R_2)$$

$$V_{R_2} = \left(\frac{V_{cc}}{R_1 + R_2} \right) (R_2)$$

$$V_{R_2} = \left(\frac{R_2}{R_1 + R_2} \right) (V_{cc})$$

$$\text{So, } V_+ = V_{R_2} = \left(\frac{R_2}{R_1 + R_2} \right) V_{cc}$$

$$V_- = V_{R_3}$$

$$V_{R_3} = (\text{Current through } R_3)(\text{resistance})$$

$$V_{R_3} = (I')(R_3)$$

$$V_{R_3} = \left(\frac{V_{cc}}{R_L + R_3} \right) (R_3)$$

$$V_{R_3} = \left(\frac{R_3}{R_L + R_3} \right) (V_{cc})$$

$$V_- = V_{R_3} = \left(\frac{R_3}{R_L + R_3} \right) (V_{cc})$$



(Question #3)

(NAND gate as NOT gate)

Diagram:



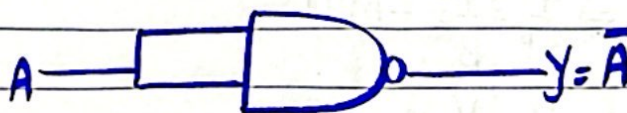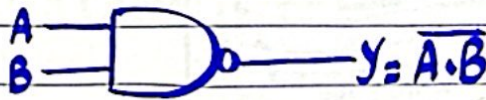We can make NOT gate from NAND gate by joining the two input terminals of NAND gate to form a single input terminal of NOT gate, and output of NOT gate is taken from output terminal of NAND gate.



Truth table:

A	B	$Y = (\overline{A \cdot B}) = \bar{A}$
0	0	1
1	1	0



Question #4)

Given:

$$\text{Collector current} = I_c = 10\text{mA} = 0.01\text{A}$$

$$\text{Current gain} = \beta = 100$$

$$\text{base-emitter voltage} = V_{BE} = 0.6\text{V}$$

To find:

$$\text{Base resistance} = R_B = ?$$

Formula:

$$V_{CC} = V_{R_B} + V_{BE}$$

$$V_{CC} = I_B R_B + V_{BE} \quad (V_{R_B} = I_B R_B)$$

$$V_{CC} - V_{BE} = I_B R_B$$

$$\frac{V_{CC} - V_{BE}}{I_B} = R_B$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} \quad \text{--- (1)}$$

$$\text{Using } \beta = \frac{I_c}{I_B} \Rightarrow I_B = \frac{I_c}{\beta} \quad \text{--- in (1)}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{V_{CC} - V_{BE}}{I_c / \beta}$$

$$R_B = \left(\frac{V_{CC} - V_{BE}}{I_c} \right) \beta$$

$$\text{Calculations: } R_B = \left(\frac{V_{CC} - V_{BE}}{I_c} \right) \beta$$


$$= \left(\frac{9 - 0.6}{0.01} \right) \times 100 = 84000 \Omega = 84\text{k}\Omega$$

Result: Base resistance is $84\text{k}\Omega$ or 84000Ω .

Question #5

$$\underline{X = (A + \bar{B})(\bar{A} + B)}$$

Diagram:

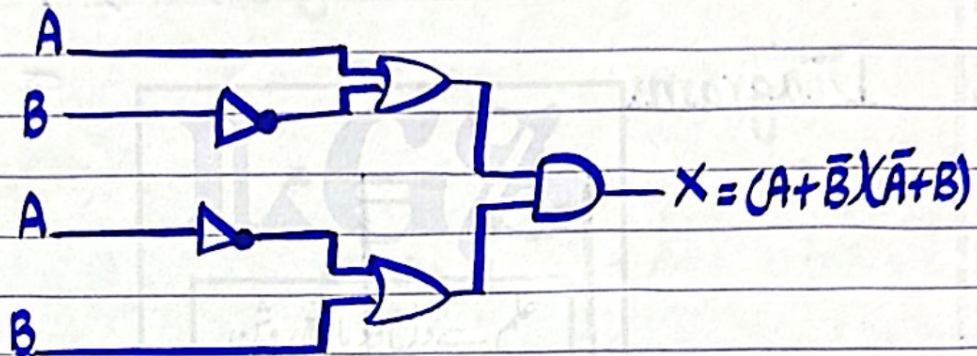

Truth table:


A	B	\bar{A}	\bar{B}	$\bar{A}B$	$A\bar{B}$	X
0	0	1	1	1	1	1
0	1	1	0	1	0	0
1	0	0	1	0	1	0
1	1	0	0	1	1	1



Question #6)

(Pressure & Temperature Control System)

Diagram:

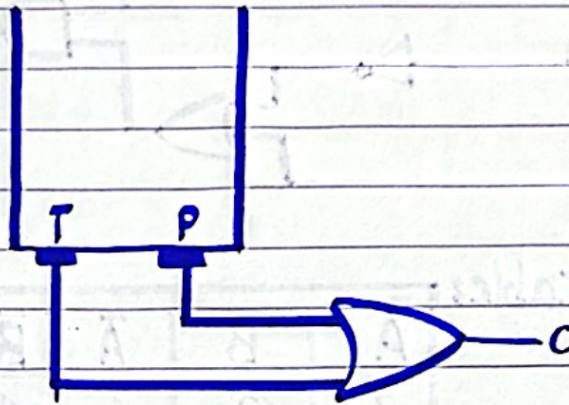

Truth table:

P	T	C
0	0	0
0	1	1
1	0	1
1	1	1