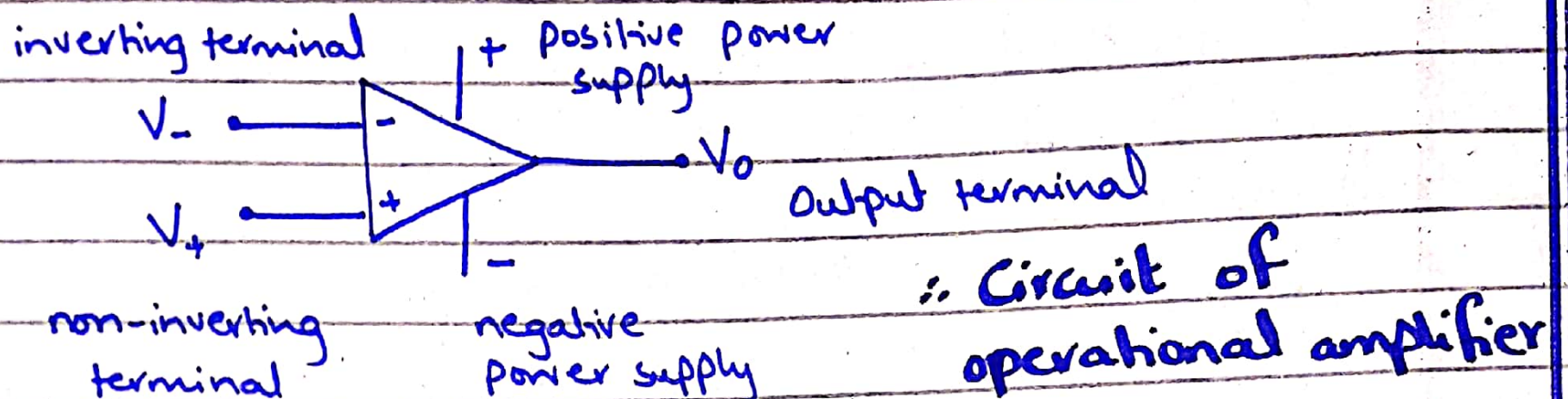


"Physics Assignment - Week 8"

"Subjective Type"

Ans Q1



Proof:

Consider an operational amplifier with V_+ as grounded
So $V_+ \approx 0$,

Also using $A_{OL} = \frac{V_o}{V_+ - V_-} \rightarrow V_+ - V_- = \frac{V_o}{A_{OL}}$

$$V_+ - V_- = \frac{V_o}{10^5} = \frac{V_o}{\text{very high value}} \approx 0$$


$$V_+ - V_- \approx 0$$

$$V_+ \approx V_- \text{ or } V_- \approx V_+$$

So V_+ is particularly grounded and V_- is virtually grounded because of its equality with V_+ .

Ans Q2

Circuit of OP amp as night switch :-

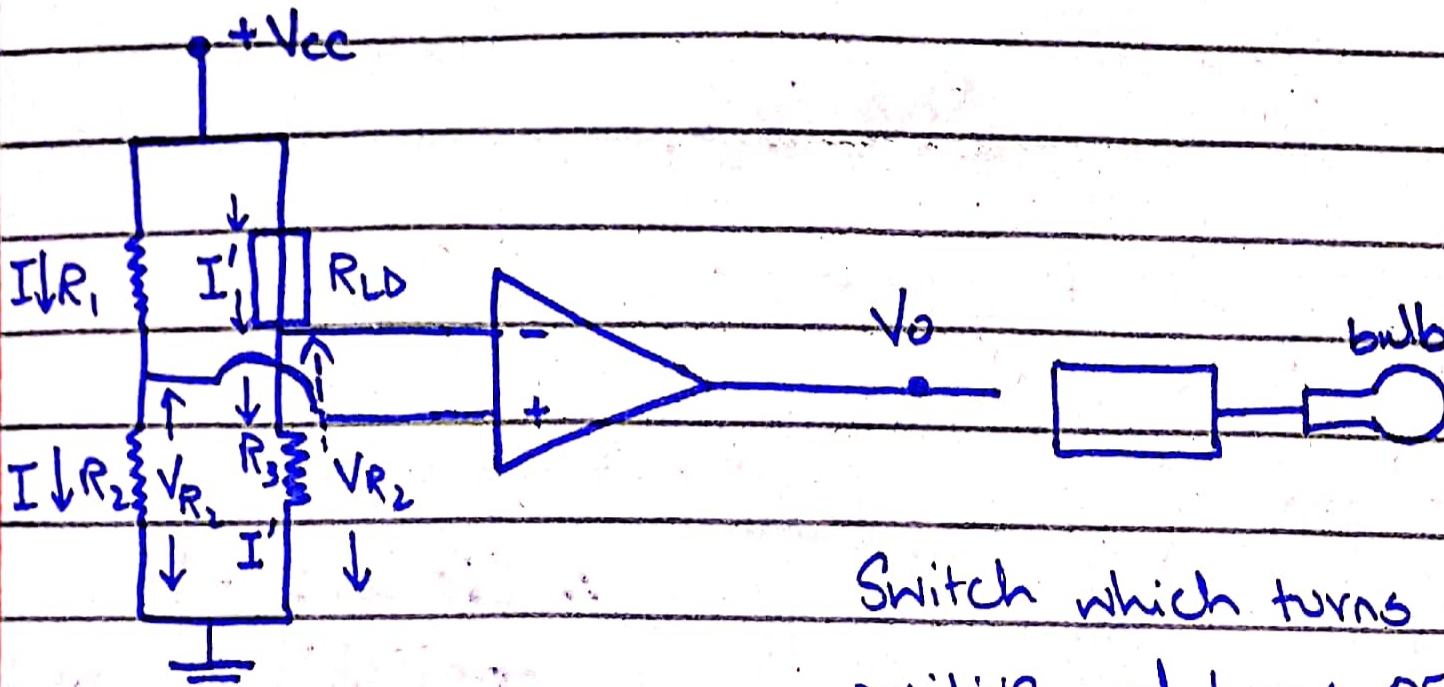

Switch which turns ON at positive and turns OFF at negative potential.

Expression of V_- and V_+ :-

During day, intensity of light high and $R_{LD} = \text{low}$

$V_- = \text{greater}$, $V_- > V_+$, $V_o = -V_{cc}$ (OFF switch)


At evening, intensity of light is low and $R_{LD} = \text{high}$

$V_- = \text{less}$, $V_+ > V_-$, $V_o = +$ (ON switch)

Ans Q3

NAND Gate :-

$$X = \overline{A \cdot B}$$

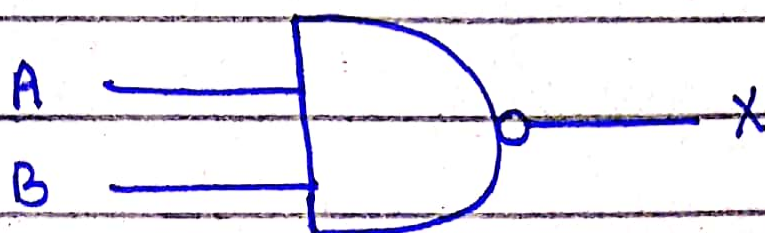

Truth Table

A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Ans Q4

Numerical :-

Given :

collector current = $I_c = 10\text{mA} = 0.01\text{A}$

current gain = $\beta = 200$

base-emitter voltage = $V_{BE} = 0.6\text{V}$

To Find :

Base-resistance = $R_B = ?$

Solution :

Using Formula,

$$V_{CC} = V_{R_B} + V_{BE}$$

$$\therefore V_{R_B} = I_B R_B$$

$$V_{CC} = I_B R_B + V_{BE}$$

$$V_{CC} - V_{BE} = I_B R_B$$

$$\frac{V_{CC} - V_{BE}}{I_B} = R_B \quad \text{--- (1)}$$

$$\text{Using } \beta = \frac{I_c}{I_B} \rightarrow I_B = \frac{I_c}{\beta} \text{ in eq (1)}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} \rightarrow \frac{V_{CC} - V_{BE}}{I_C / \beta} \rightarrow R_B = \left(\frac{V_{CC} - V_{BE}}{I_C} \right) \beta$$


$$R_B = \left(\frac{9 - 0.6}{0.01} \right) \times 200 = 168000 \Omega = 168 \text{ k}\Omega$$

Base resistance is $168 \text{ k}\Omega$.

Ans Q5

Boolean diagram and Truth table of $X = (A + \bar{B})(\bar{A} + B)$:-

→ Diagram

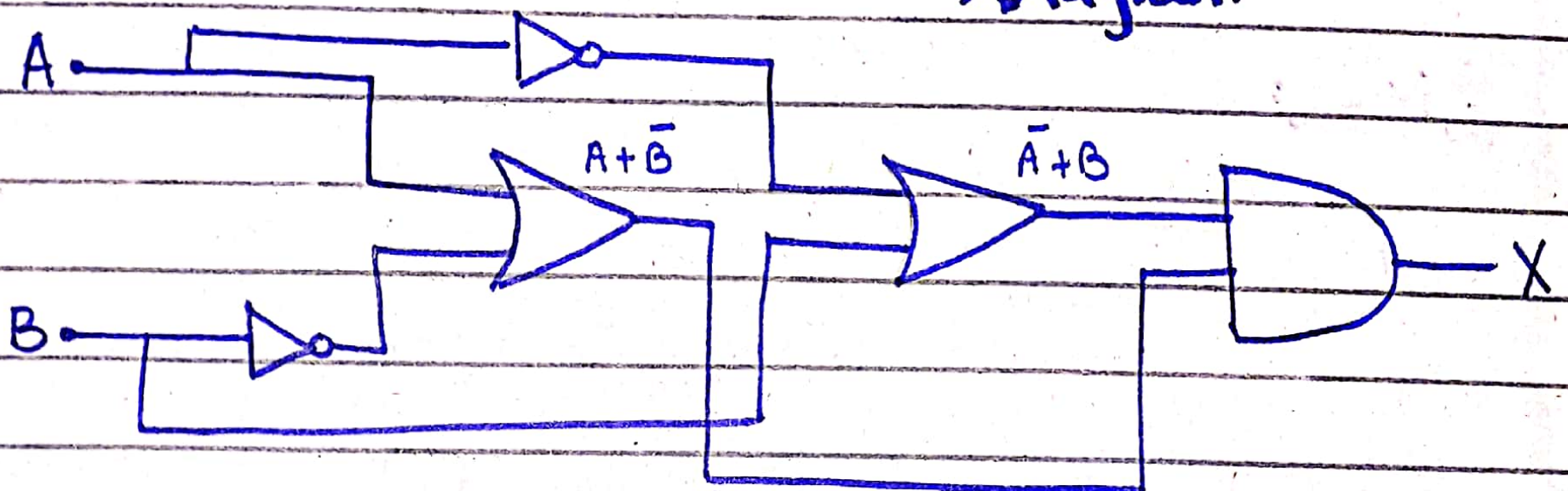


A	B	\bar{A}	\bar{B}	$A + \bar{B}$	$\bar{A} + B$	$A + \bar{B} \cdot \bar{A} + B$
0	0	1	1	1	1	1
0	1	1	0	0	1	0
1	0	0	1	1	0	0
1	1	0	0	1	1	1

→ Truth Table

Ans Q6

Diagram of a boiler :-

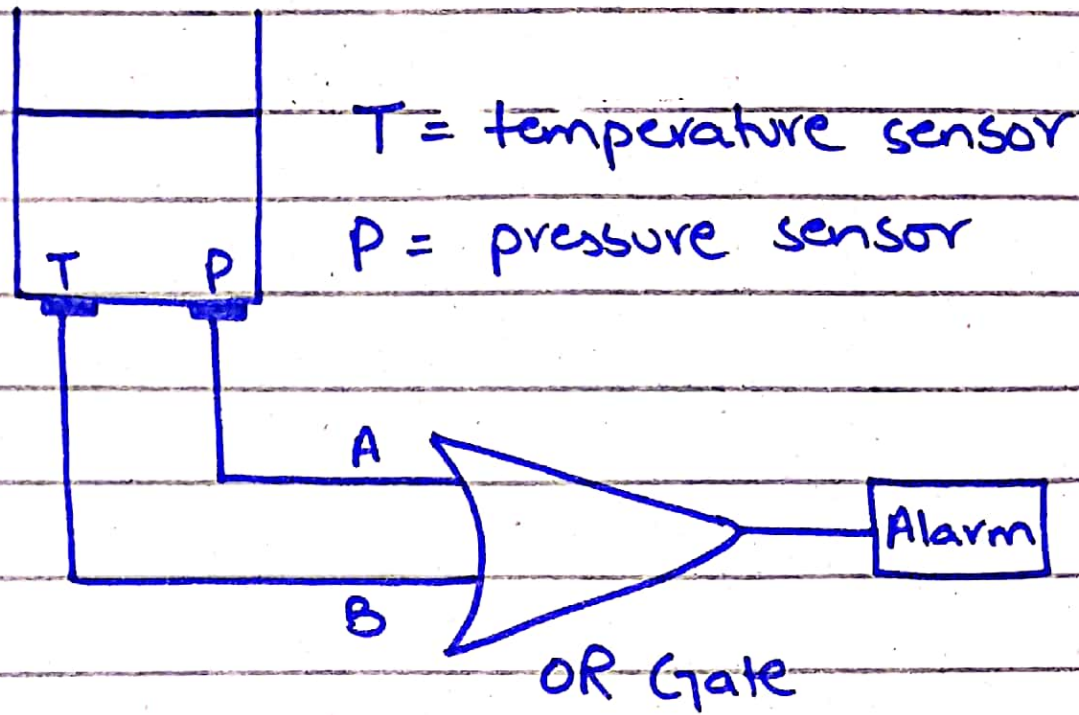

Truth table :

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1