


Name : Subhan Nadeem

Physics

Subjective Type

Question: 3

Relation between I & V in inductor:

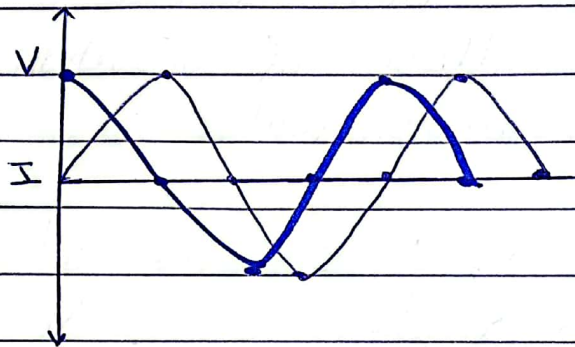

- 1) Voltage leads by current with 90° or $\frac{\pi}{2}$ rad
OR
- 2) Current lags behind voltage with 90° or $\frac{\pi}{2}$ rad

Question: 4

Frequencies of A.M & F.M

A.M:

It has small frequency range from 540 KHz to 1600 KHz

Where As

F.M

It has large frequency range from 88 MHz to 108 MHz .



Question: 6

Choke coil:

Choke: is a coil of thick copper wire wound closely in large number of turns over a soft iron core.

Use:

It is used in A.C circuits to limit the current with extremely small wastage of energy.

Question: 7

Sol:

$$\text{inductance} = L = 20 \text{ mH} = 0.02 \text{ H}; R = 10 \Omega$$

$$\text{voltage} = 240 \text{ V}; f = 180/\pi$$

Formula:

$$P = VI \cos \phi$$

$$P = V \left(\frac{V}{Z} \right) \left(\frac{R}{Z} \right) \Rightarrow P = \frac{V^2 R}{Z^2} \Rightarrow \frac{V^2 R}{[\sqrt{R^2 + X_L^2}]^2}$$

$$P = \frac{V^2 R}{R^2 + 4\pi^2 f^2 L^2}$$

$$R^2 + 4\pi^2 f^2 L^2$$

Put values

$$P = \frac{(240)^2 \cdot (10)}{(10)^2 + 4\pi^2 \left(\frac{180}{\pi} \right)^2 (0.02)^2} \Rightarrow \frac{576000}{100 + 51.84}$$

$$P = 3793.4 \text{ W}$$

Question: 6

Information

1) The actual message or signal to be transmitted.

Carrier

1) A high frequency signal that carries "the information" on signal over communication line.



Question: 1

The frequency response of capacitor is opposite to inductor. We know frequency in C when connected to A.C is:

Capacitor

$$f \propto \frac{1}{X_C}$$


Inductor:

$$f \propto X_L$$

So, in Capacitor X_C is inversely to F and in inductor X_L is directly.

Question: 2

Impedance diagram:

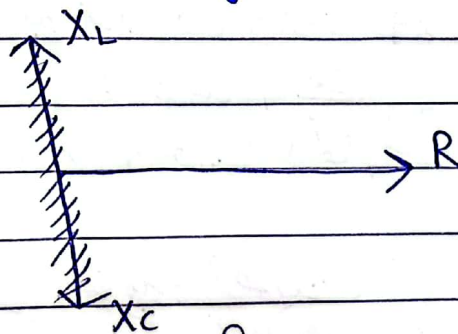

As at resonance frequency $X_L = X_C$ so cancelled and both are in phase \angle so power factor is $(\cos 0^\circ)$ is 1.