



**Date: 18-11-2024**

# LGS GROUP OF COLLEGES

**Physics**

**Assignment**

**XII (A)**

**TEST#**

**WK-8**


<b>Topic:</b> 18.7 to 18.14	<b>Name:</b> .....	<b>Roll No:</b>					
<b>Time:</b> 35 mins		<b>Marks =15</b>					

Q1. Draw a circuit of OP amp and show that under virtual ground conditions  $V_-$  and  $V_+$  are approximately equal. (02)

Q2. Draw circuit diagram of OP amp as night switch and write down the expressions of  $V_-$  and  $V_+$ . (02)

Q3. How a NAND gate can be used as NOT gate, draw diagram and truth table. (02)

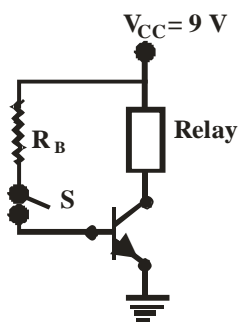Q4. Fig. shows a transistor which operates a relay as the switch S is closed. The relay is energized by a current of 10 mA. Calculate the value  $R_B$  which will just make the relay operate. The current gain  $\beta$  of the transistor is 100. When the transistor conducts, its  $V_{BE}$  can be assumed to be 0.6 V. (03)



Q5. Draw Boolean diagram and truth table of  $X = (A + \bar{B})(\bar{A} + B)$ . (03)

Q6. Draw a pressure and temperature control system of a boiler with the help of OR gate with help of diagram and truth table. (03)