



Physics Assignment


Week 8

Short Questions

Q₁

Operating amplifier is used as an inverting configuration under virtual ground conditions. Under ideal conditions $V_i \approx V$ if $V_+ = 0$, the virtual ground ensures $V_- = 0$.

$$I_{in} = I_f$$

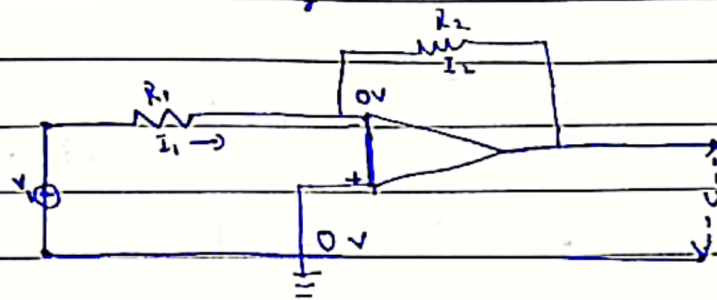Q₃

Connect both inputs of NAND gate together ($A = B$).

A	Output (Y) = $\bar{A} \cdot \bar{A} = \bar{A}$
0	1
1	0

NAND gate behaves like a not gate.

Q₄

Given :-

$$V_{CC} = 9V, I_C = 10\mu A, \beta = 100, V_{BE} = 0.6V$$

Sol:-

$$I_B = \frac{I_C}{\beta} = \frac{10 \times 10^{-3}}{100} = 0.1 \text{ mA}$$


$$V_{RB} = V_{CC} - V_{BE} = 9 - 0.6 = 8.4 \text{ V}$$

$$R_B = \frac{V_{RB}}{I_B} = \frac{8.4}{0.1 \times 10^{-3}} = 84 \text{ k}\Omega$$

Q5


Truth table

A	B	A+B	A+B	$X = (A+B)(\bar{A} + \bar{B})$
0	0	0	1	0
0	1	1	1	1
1	0	1	0	0
1	1	1	1	1

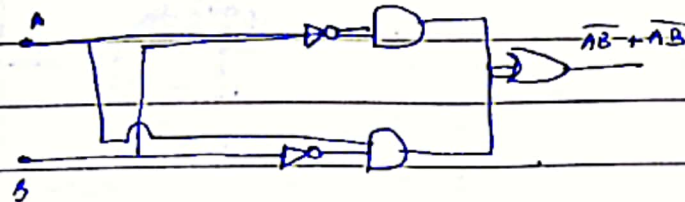

Q6

P	T	output
0	0	0
0	1	1
1	0	1
1	1	1

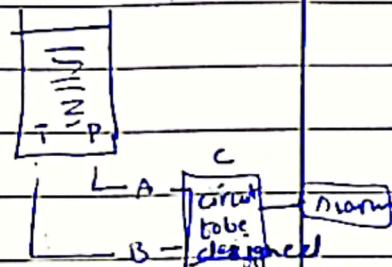

Q2

